

- The instantaneous value of alternating emf is given by

$$E = E_0 \sin \omega t$$

Where,

$E_0 \rightarrow$ Peak value of alternating emf

$\omega t \rightarrow$ Phase of alternating emf

Similarly, the instantaneous value of alternating current is given by

$$I = I_0 \sin \omega t$$

Where, $I_0 \rightarrow$ Peak value of alternating current

- The average value or mean value of alternating current over half cycle is given by


$$I_m = \frac{2}{\pi} I_0$$

- The root mean square value (rms value) or virtual value of AC is given by

$$I_v = \frac{I_0}{\sqrt{2}}$$

- AC through a resistor:**

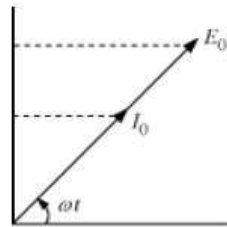When AC flows through a resistor, the voltage and current are in phase with each other.




Phasor diagram

- AC through an inductor:**

The alternating emf is ahead of alternating current by a phase angle of $\frac{\pi}{2}$.

Inductive reactance (X_L):

$$X_L = \omega L = 2\pi fL$$

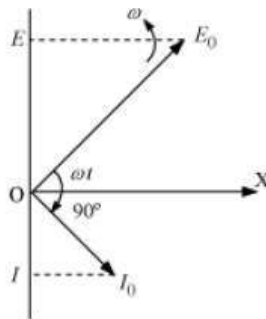


- AC through a capacitor:**



The current leads the emf by a phase angle of $\frac{\pi}{2}$.

Capacitive reactance (X_C):
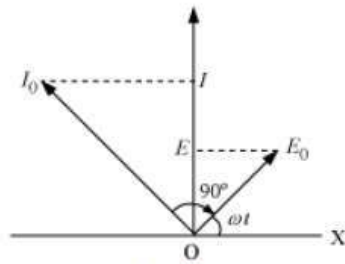
$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$




- AC through LR circuit:

$$E = I\sqrt{R^2 + X_L^2}$$


Inductive impedance (Z_L) of LR circuit:

$$Z_L = \sqrt{R^2 + X_L^2}$$
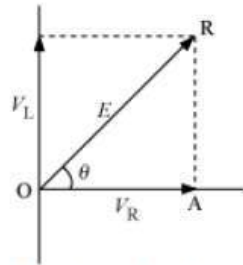
$$\tan \phi = \frac{X_L}{R} = \frac{\omega L}{R}$$



- AC through CR circuit:

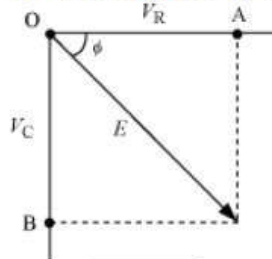


$$E = I\sqrt{R^2 + X_C^2}$$

Capacitive impedance:

$$Z_C = \sqrt{R^2 + X_C^2}$$

- AC through LCR series circuit:



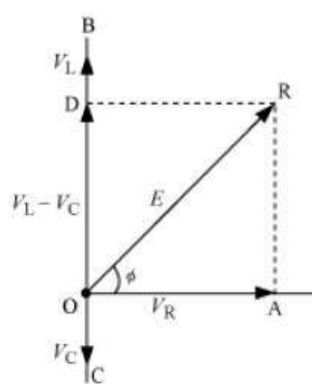

$$E = I\sqrt{R^2 + X_L - X_C^2}$$

$$\tan\phi = \frac{X_L - X_C}{R}$$

Impedance (Z):

$$Z = \sqrt{R^2 + X_L - X_C^2}$$

- **Power in LCR circuit:**

$$P_{av} = \frac{E_V^2 R}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\text{Power factor} = \cos\phi = \frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

- **Resonance:**

An interesting characteristic of a series LCR circuit is the phenomenon of resonance. The amplitude of the current is the maximum at the resonant

frequency, $\omega_0 = \frac{1}{\sqrt{LC}}$

- **Quality factor:**

The quality factor Q , defined by $Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$, is an indicator of the sharpness of the resonance.

- A transformer consists of an iron core, on which are bound a primary coil of N_p turns and a secondary coil of N_s turns. If the primary coil is connected to an AC source, the primary and secondary voltages are related by

$$V_s = \left(\frac{N_s}{N_p}\right) V_p$$

And the currents are related by $I_s = \left(\frac{N_p}{N_s}\right) I_p$

If $N_s > N_p \rightarrow$ The voltage is stepped up (step-up transformer)

If $N_s < N_p \rightarrow$ The voltage is stepped-down (step-down transformer)